
Energy Efficient Nanoelectronic System Design

Saraju P. Mohanty

NanoSystem Design Laboratory (NSDL)

Dept. of Computer Science and Engineering

University of North Texas, Denton, TX 76203, USA.

Email: saraju.mohanty@unt.edu

A green light to greatness.

05/21/2013





UNT

Outline of the Talk

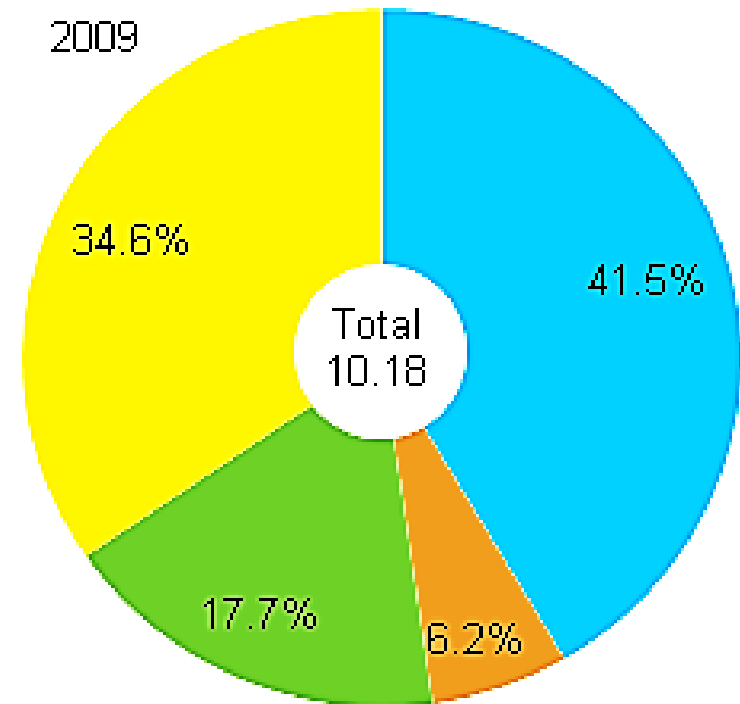 - Example Consumer Electronic Systems
- Typical Electronic System Components
- The Power Issue: In a Nanoelectronic System
- Options for Energy Efficient System Design
- Conclusions and Future Research

Consumer Electronics Demand More and More Energy

Energy consumption in homes by end uses
quadrillion Btu and percent



■ space heating ■ air conditioning ■ water heating ■ appliances, electronics, and lighting

Quadrillion BTU (or quad): 1 quad = 10^{15} BTU = 1.055 Exa Joule (EJ).

Source: U.S. Energy Information Administration.

A green light to greatness.



UNT

Electronic System: Smart Phone



- Smarter ... Faster ... High Throughput ...
→ Power Hungry !! Battery Hungry !!

A green light to greatness.



UNT[®]

Electronic System: Many Others (Same Story)



- Smarter ... Faster ... High Throughput ...
→ Power Hungry !! Battery Hungry !!

A green light to greatness.



UNT

Battery Dependency: Not Overstated



One 787 Battery:
12 Cells / 32 V DC



- Boeing 787's across the globe were grounded.

Source: <http://www.newairplane.com>


A green light to greatness.

05/21/2013




UNT[®]

Why Energy Efficient Design ?

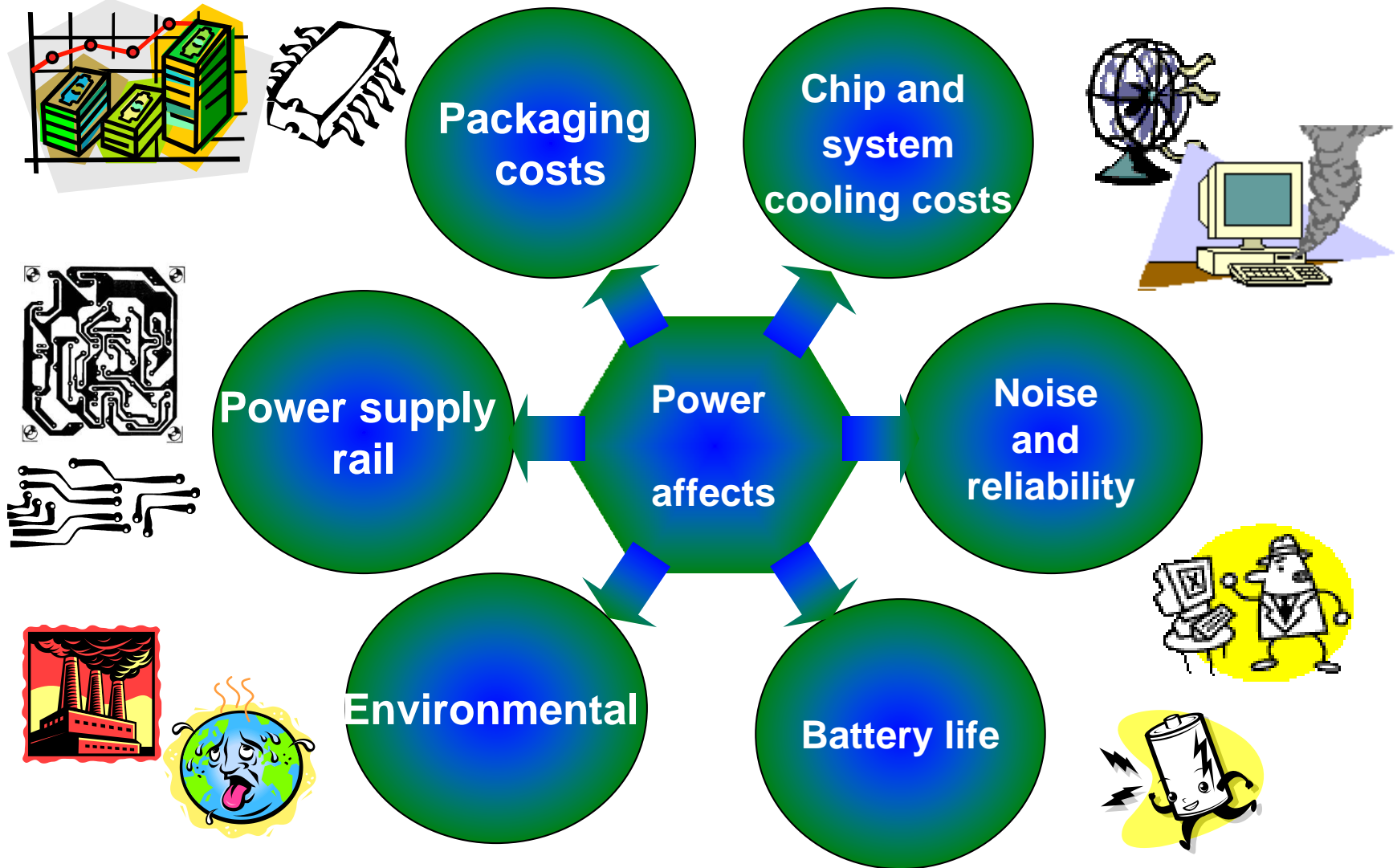

A green light to greatness.

A Typical Electronic System

 


- Consists of several heterogeneous components.

A green light to greatness.

A Typical Electronic System: Where Energy Consumed??


Power of a Mobile System (in mW)

 

Power dissipation breakdown in idle mode of a
connected mobile device

Source: Pering MobiSys 2006

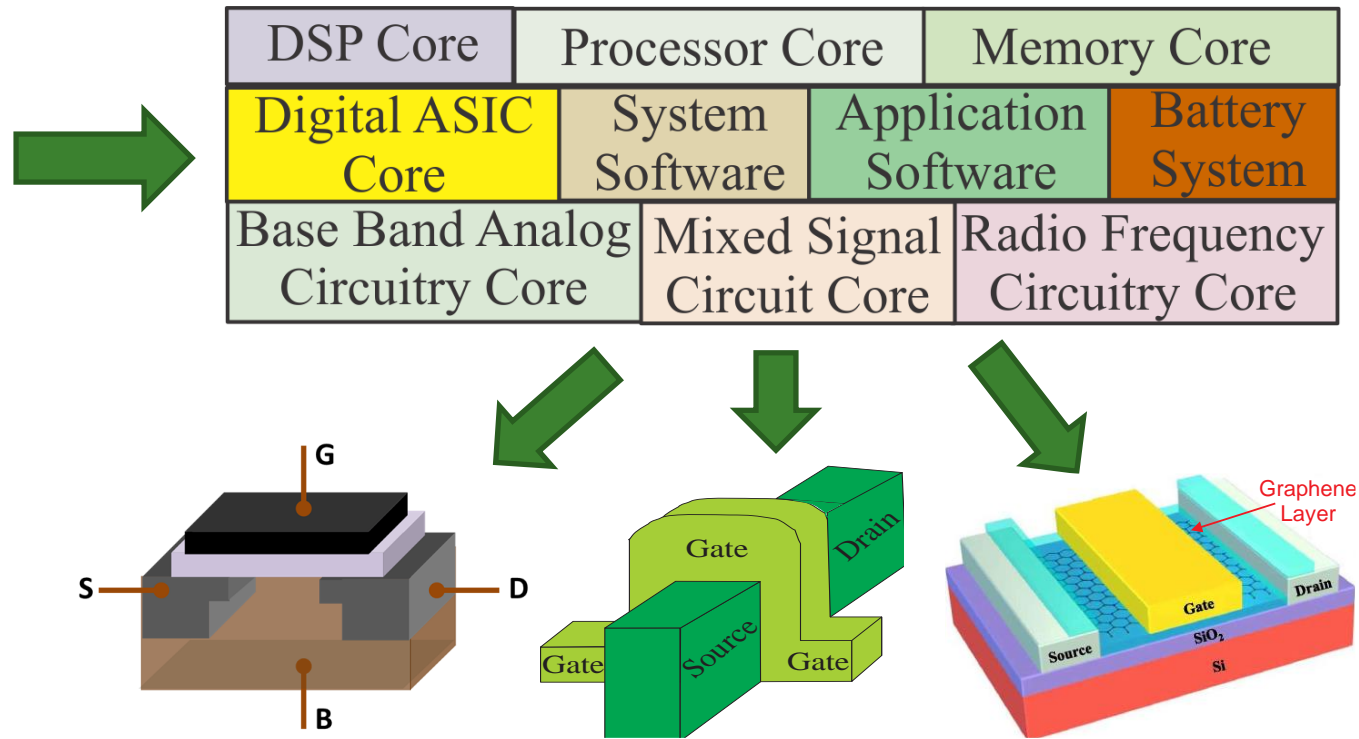A Typical Nanoelectronic System: (Many Diverse Components)




- Components have millions of nanoscale transistors.

A green light to greatness.




UNT

Nano-CMOS: Transistor Currents

 


- I_1 : drain-to-source active current (ON state)
 - I_2 : drain-to-source short circuit current (ON state)
 - I_3 : subthreshold leakage (OFF state)
 - I_4 : gate Leakage current (both ON & OFF states)
 - I_5 : gate current due to hot carrier injection (both ON & OFF states)
 - I_6 : channel punch through current (OFF state)
 - I_7 : gate induced drain leakage (OFF state)
 - I_8 : band-to-band tunneling current (OFF state)
 - I_9 : reverse bias PN junction leakage (both ON & OFF states)
- Source: Mohanty Book 2008

Nano-CMOS: Power Dissipation Types

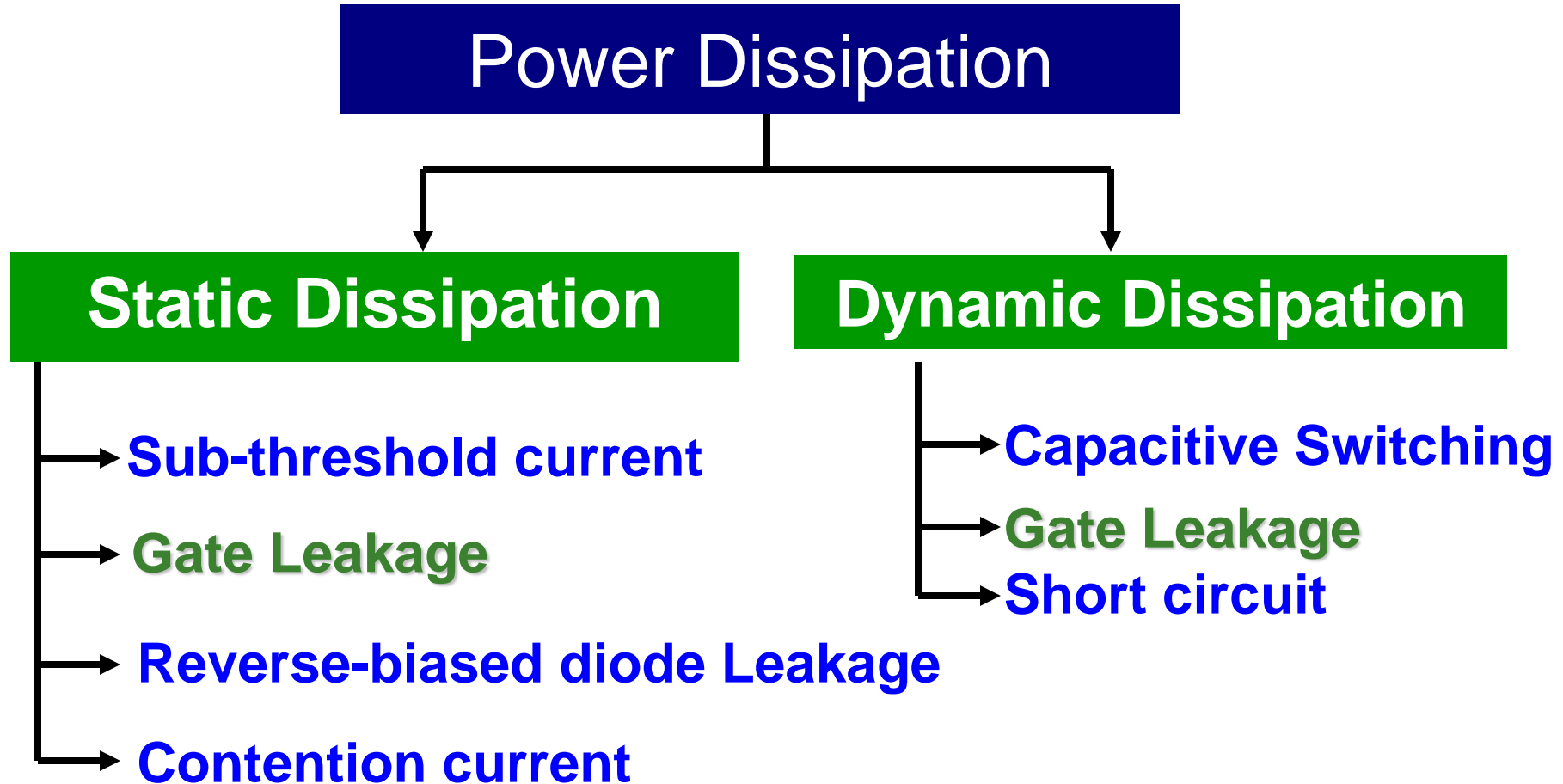

Source: Mohanty Book 2008

Nano-CMOS: Power Dissipation Trend

 


Source: Mohanty Book 2008

A green light to greatness.



UNT

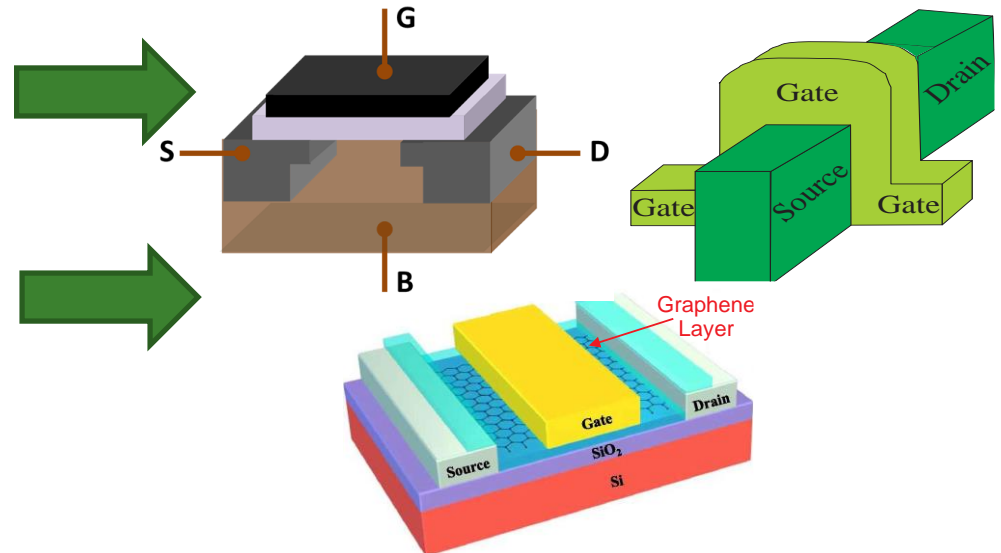
A Typical Nanoelectronic System: Research Questions



■ Questions:

- How to perform energy-efficient designs.
- How to perform high-yield, energy efficient designs.
- How to perform effortless, high-yield, energy efficient designs.

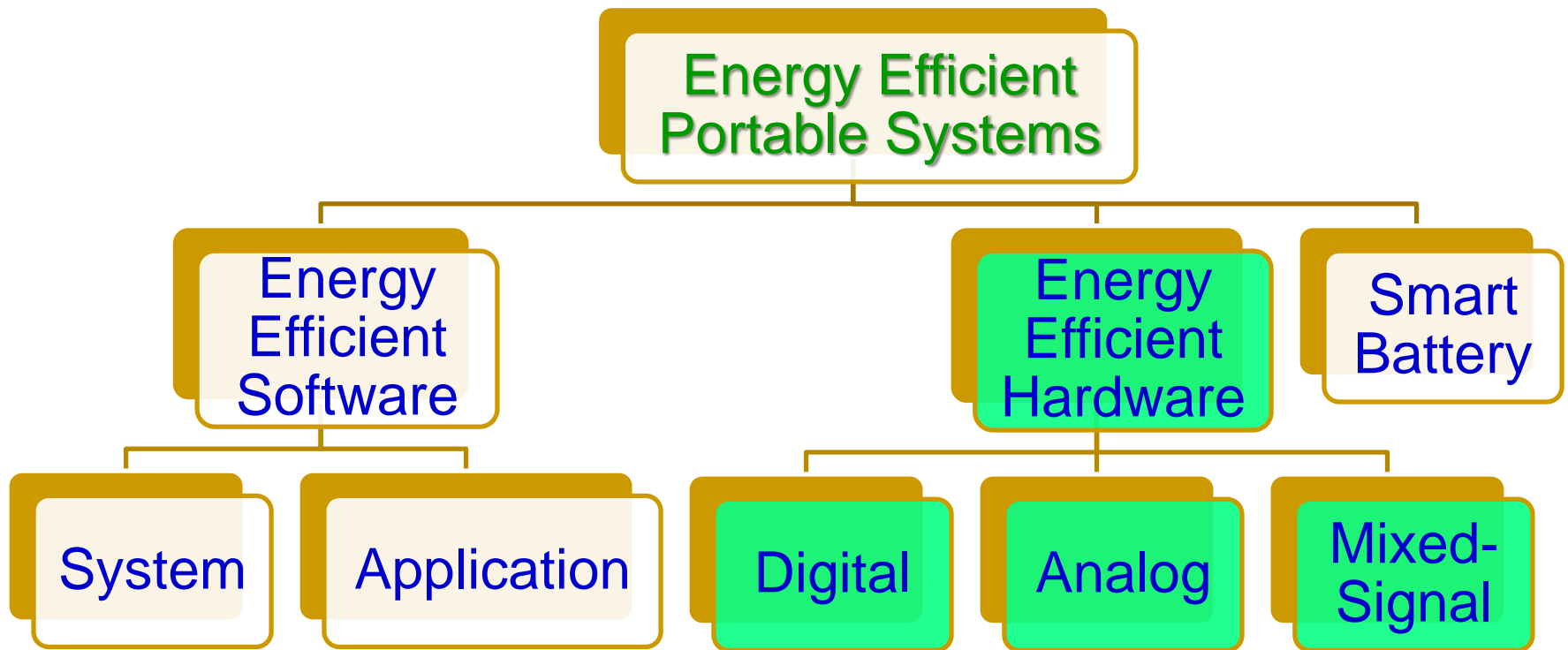
Energy Efficient Nanoelectronic Systems: Possible Solution Fronts



Energy Efficient Hardware -- 1

- Design of an Universal Level Converter for Dynamic Power Management
- S. P. Mohanty, E. Kougianos, and O. Okobiah, “Optimal Design of a Dual-Oxide Nano-CMOS Universal Level Converter for Multi-V_{dd} SoCs”, *Springer Analog Integrated Circuits and Signal Processing Journal*, Vol. 72, No. 2, August 2012, pp. 451--467.

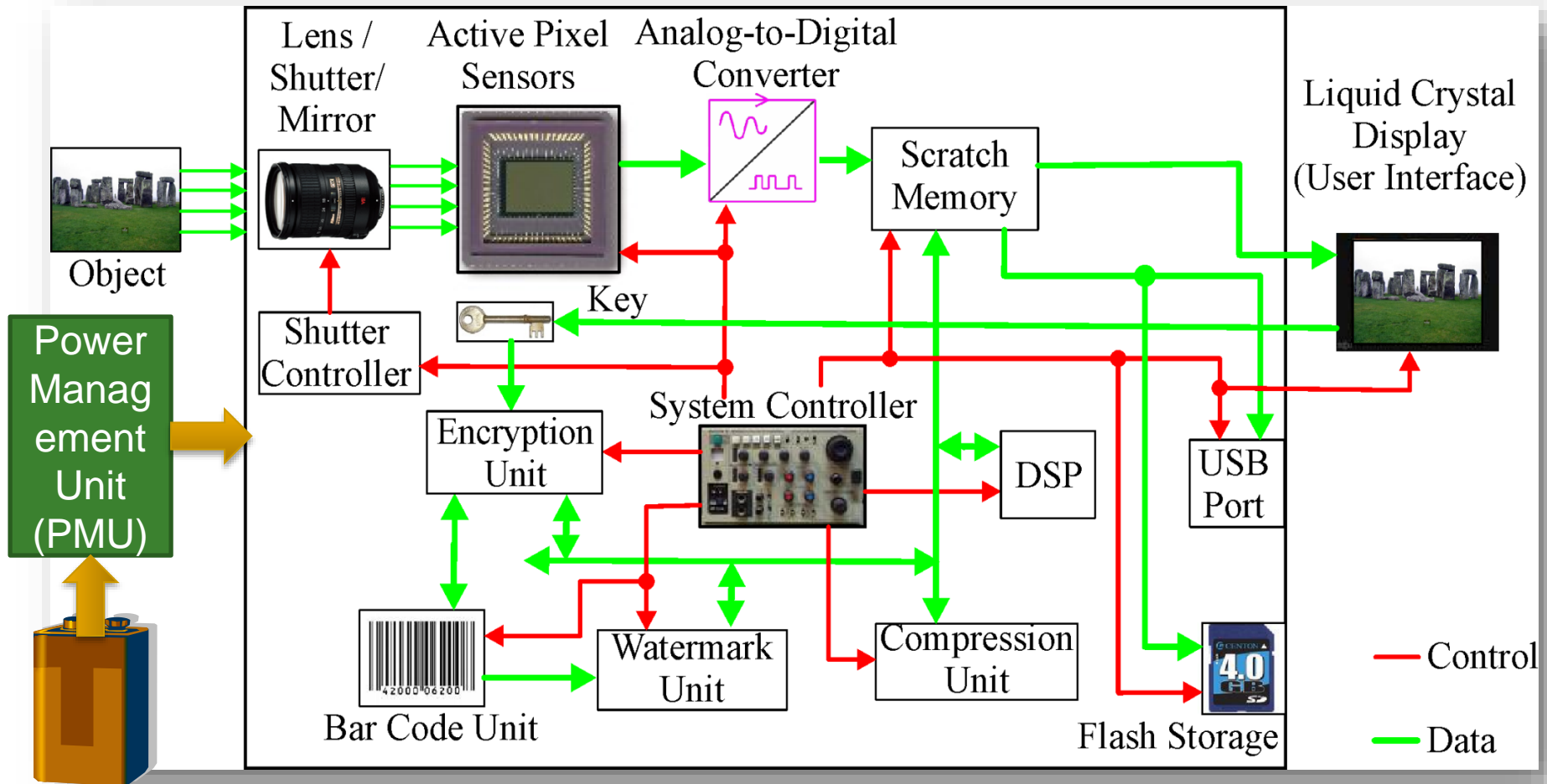One Example Electronic System: Secure Digital Camera




A green light to greatness.


Power Management Unit (PMU)

- Manages the power distribution to the various subsystems to optimize energy consumption.
- Has built-in timers that put the different components to “sleep” or “wake-up”.
- The heart of PMU is a bank of Universal Voltage-Level Converters (ULCs).
- ULC sends different operating voltages to various subsystems and facilitates reconfigurability for power management.

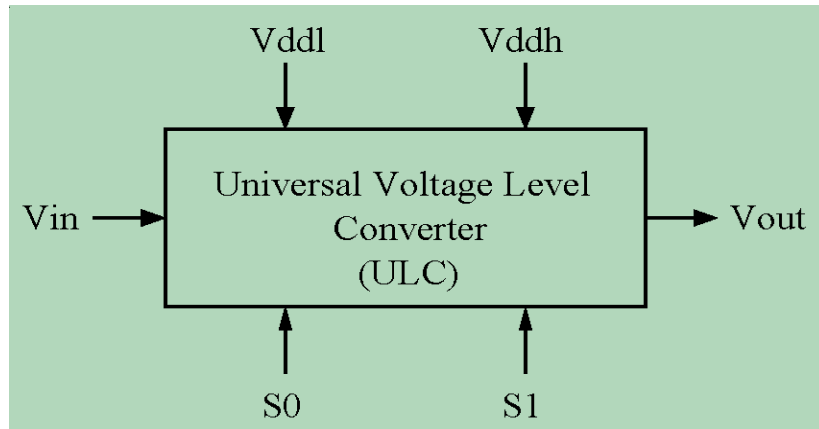
Universal Voltage-Level Converter: Use in a System



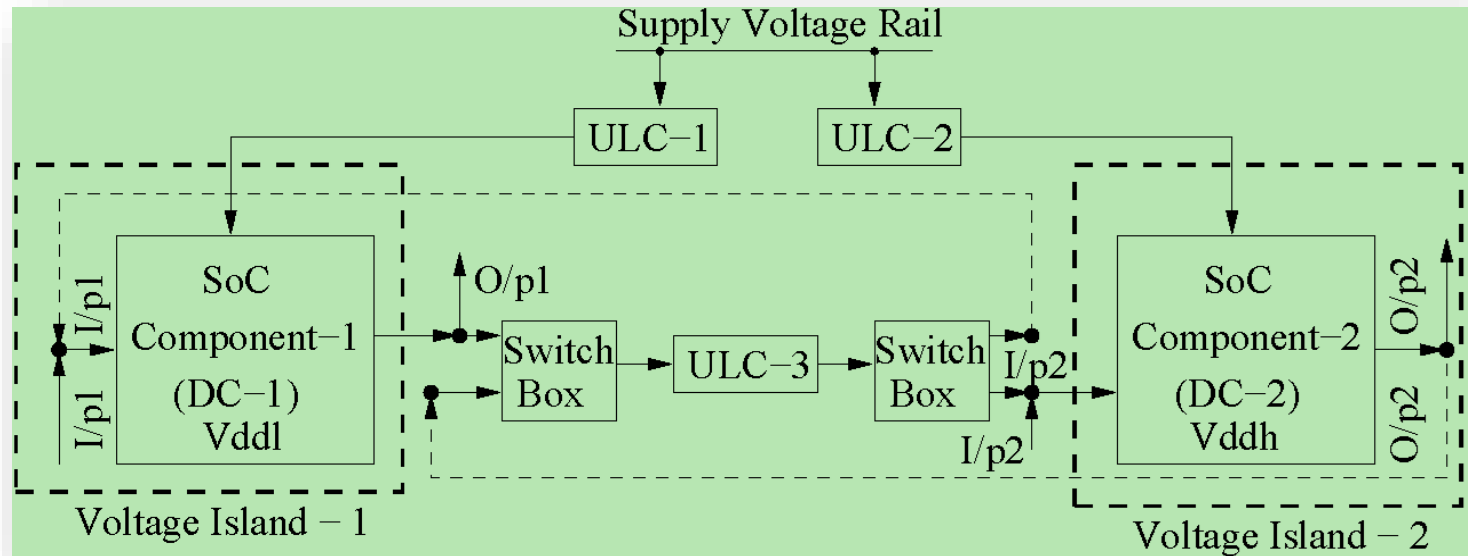- ULC Input voltage signal V_{in}
- ULC Control signals S_1 and S_0
- ULC Supply voltages V_{ddl} , V_{ddh}
- ULC Output voltage signal V_{out}




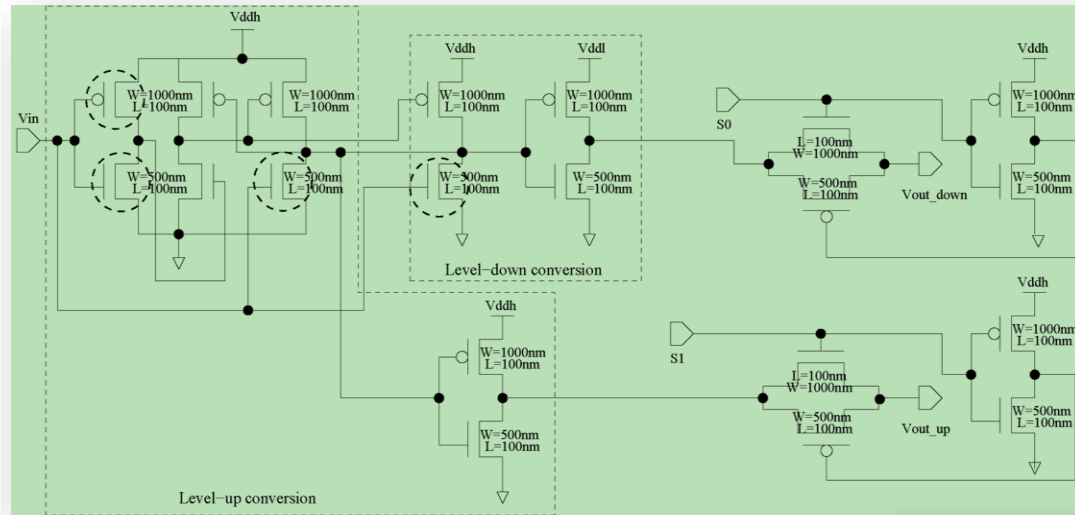Universal Voltage-Level Converter: One Topology



- 20 transistor area efficient design.
- Energy hungry transistors are circled.

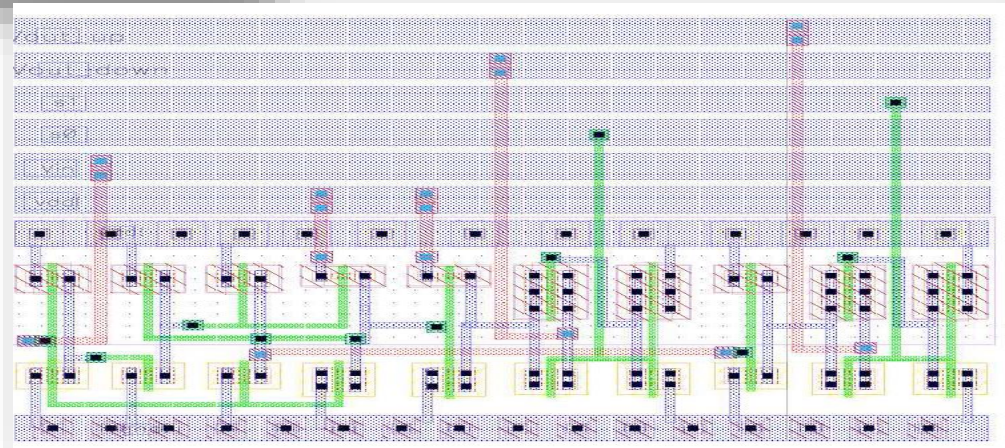- Energy hungry transistors have thicker oxide.
- 90nm CMOS dual-oxide physical design of ULC.




A green light to greatness.

Universal Voltage-Level Converter: Operations

Operations of the ULC:

- ❑ Level-up conversion
- ❑ Level-down conversion
- ❑ Blocking of input signal

Select Signal		Type of Operation
0	0	Block Signal
0	1	Up Conversion
1	0	Down Conversion

 

Output

Input

Universal Voltage-Level Converter: Has Minimal Overhead

Designs	Technology (nm)	Power	Delay	Conversion	Design Approach
Ishihara 2004	130nm	---	127 ps	Level-up and down	Level converting flip flops
Yu 2001	350nm	220.57 μ W	---	Level-up	SDCVS
Sadeghi 2006	100nm	10 μ W	1 ns	Level-up	Pass transistor and Keeper transistor
Our ULC	90 nm	12.26 μ W	113.8 ps	Level-up/down and block	All conversion types and Programmable

A green light to greatness.




UNT

Energy Efficient Hardware -- 2


- Design of Energy-Efficient Phase-Locked Loop (PLL) for Clock Generation
- O. Garitselov, S. P. Mohanty, and E. Kougianos, “Accurate Polynomial Metamodeling-Based Ultra-Fast Bee Colony Optimization of a Nano-CMOS PLL”, *Journal of Low Power Electronics*, Volume 8, Issue 3, June, 2012, pp. 317--328.

Phase Locked Loop: Application

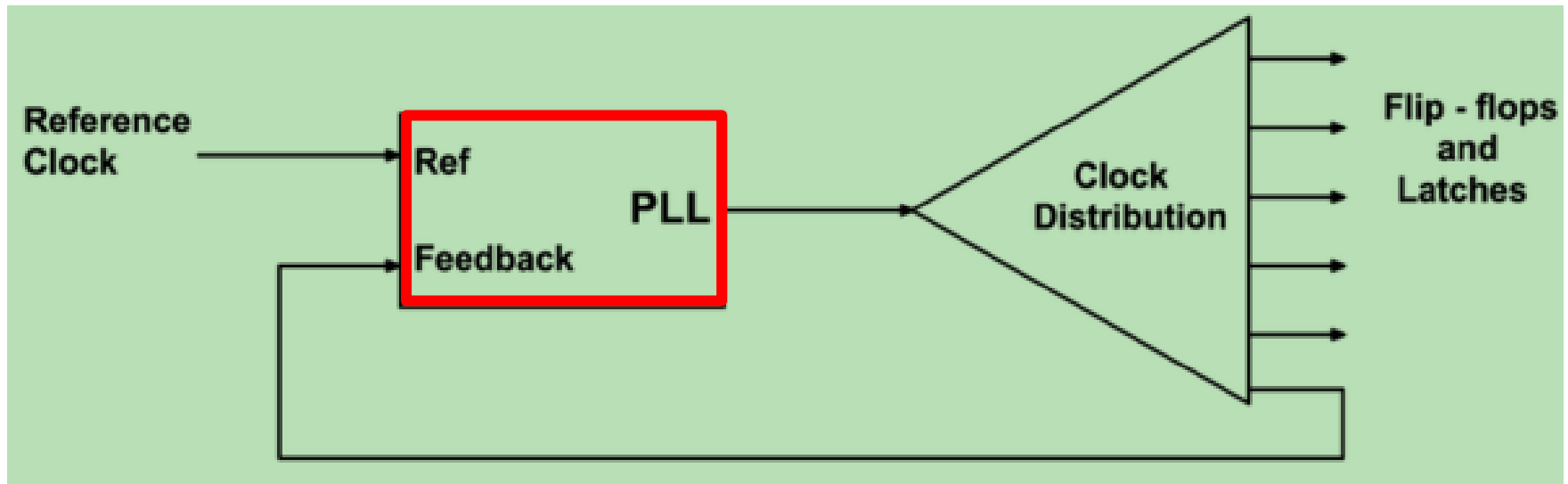


- PLLs are everywhere.
- PLLs drive clock distribution of a synchronous system.
- Sequential elements like Flip-Flop, Latches, and Registers need clock.

Phase Locked Loop: Block Diagram

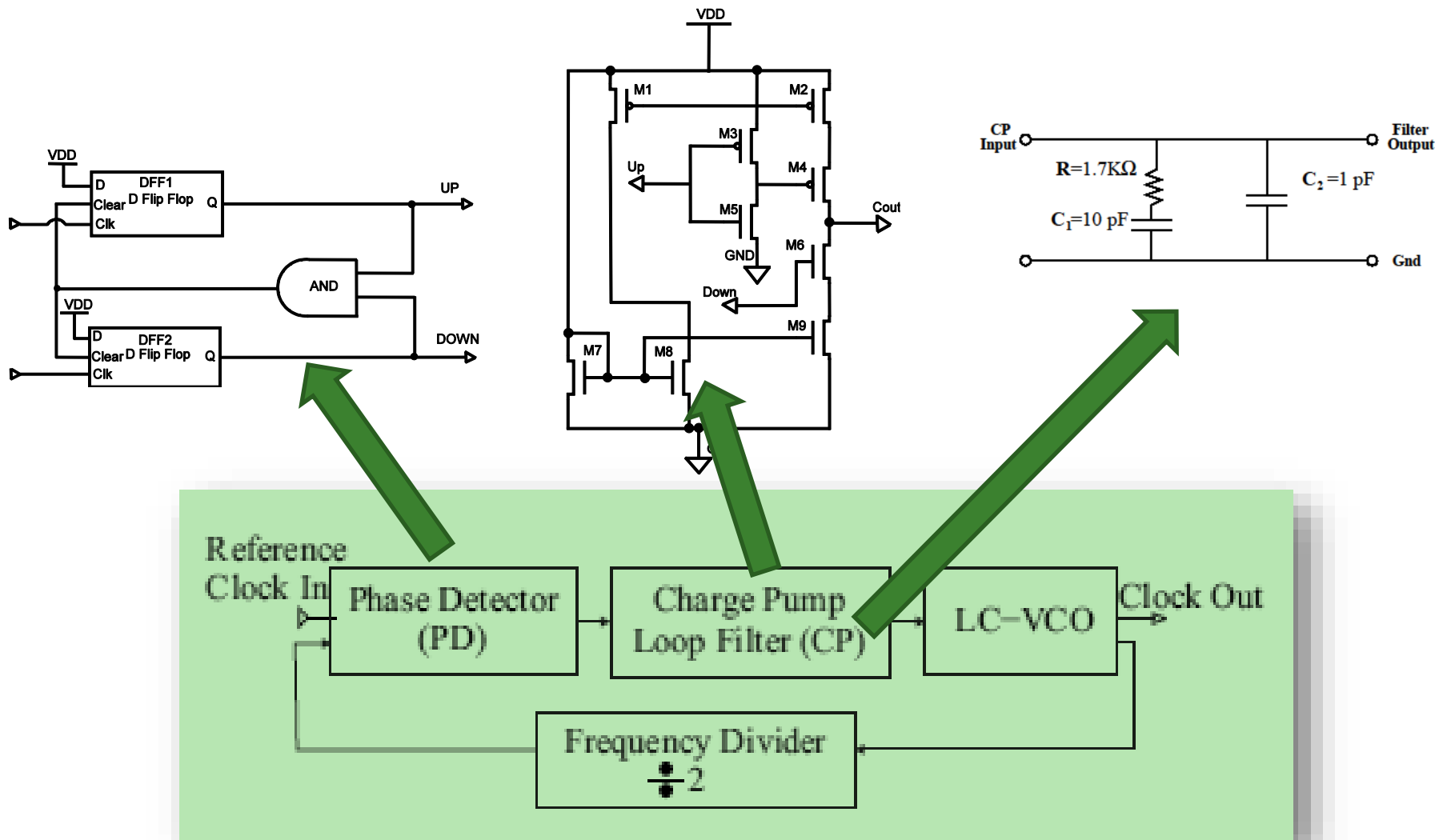

A green light to greatness.


PLL Component: 180nm LC-VCO

 


- LC-VCO oscillations are based on the sizes of L1 and C1=C2 varactors.

Schematic

Layout

 

LC-VCO Tuning Range

 


Optimization of the PLL

PLL parameters with constraints and optimized values.


Circuit	Parameter	Min (m)	Max (m)	Optimal Value (m)
Phase Detector	W_{ppd1}	400n	2μ	1.66μ
	W_{npd1}	400n	2μ	1.11μ
	W_{ppd2}	400n	2μ	784n
	W_{npd2}	400n	2μ	689n
	W_{ppd3}	400n	2μ	1.54μ
	W_{npd3}	400n	2μ	737n
Charge Pump	W_{nCP1}	400n	2μ	1.24μ
	W_{pCP1}	400n	2μ	1.35μ
	W_{nCP2}	1μ	4μ	1.35μ
	W_{pCP2}	1μ	4μ	2.88μ
LC-VCO	W_{nLC}	3μ	20μ	18.62μ
	W_{pLC}	6μ	40μ	37.48μ
Divider	W_{p1Div}	400n	2μ	1.65μ
	W_{p2Div}	400n	2μ	1.54μ
	W_{p3Div}	400n	2μ	1.38μ
	W_{p4Div}	400n	2μ	1.96μ
	W_{n1Div}	400n	2μ	1.09μ
	W_{n2Div}	400n	2μ	1.17μ
	W_{n3Div}	400n	2μ	1.29μ
	W_{n4Div}	400n	2μ	1.95μ
	W_{n5Div}	400n	2μ	536n

- An exhaustive search of the design space of 21 parameters with 10 intervals per parameter requires 10^{21} simulations.
- Time savings are enormous: $\sim 10^{20}x$.
- This can lead to reduction of design effort and chip cost.


Complete PLL : 180nm

 

PLL physical design for 180nm

 

Optimization of the PLL ...

 

Artificial Bee-Colony Optimization algorithm progression for the selected FoM.


Power and Jitter Results of the PLL

Metric	Before Optimization	After Optimization	Improvement
Power	9.29 mW	0.87 mW	90.6%
Jitter Vertical	168.35 μ V	3.28 nV	\sim 100%
Jitter Horizontal	189 ps	180 ps	4.8%

Energy Efficient Hardware -- 3


- Design of Energy-Efficient Sense Amplifier for Memory
- O. Okobiah, S. P. Mohanty, E. Kougianos, and M. Poolakkaparambil, "Towards Robust Nano-CMOS Sense Amplifier Design: A Dual-Threshold versus Dual-Oxide Perspective", in *Proceedings of the 21st ACM/IEEE Great Lakes Symposium on VLSI (GLSVLSI)*, 145--150, 2011.

Sense Amplifier : Application

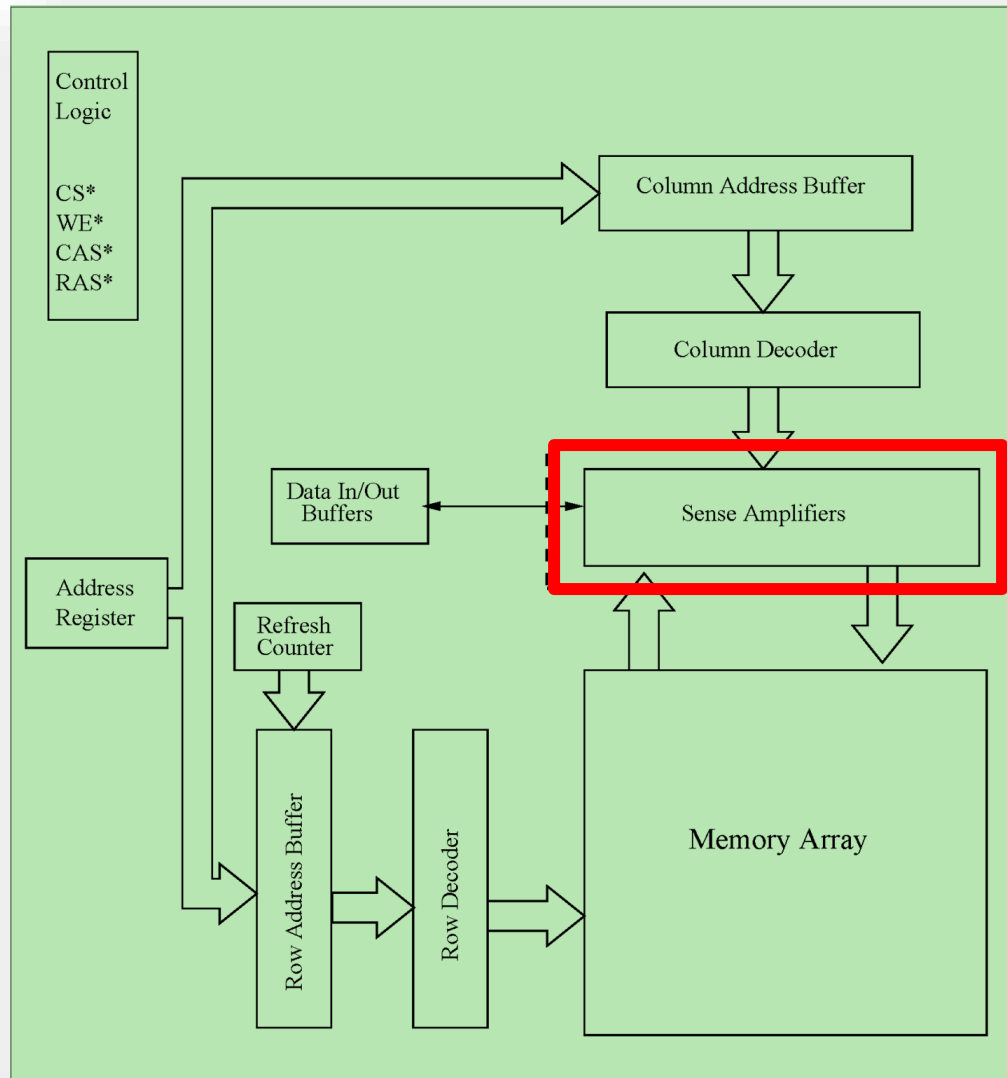


A green light to greatness.

Functional Design of Sense Amplifier

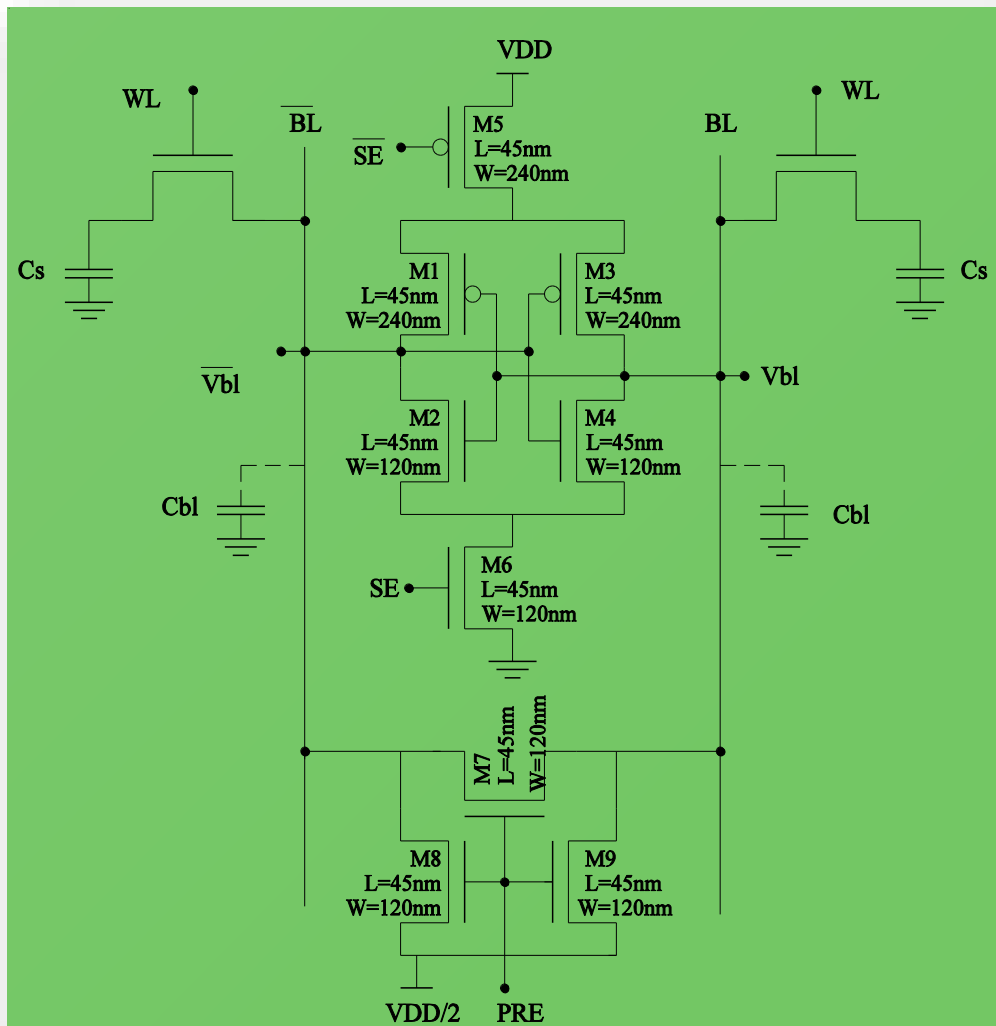


- M1, M3, M2 and M4 form cross-coupled inverters.
- M7, M8 and M9 form the precharge circuit

45nm Sense Amplifier Layout

 

- ❑ $L_n = 45\text{nm}$
- ❑ $L_p = 45\text{nm}$
- ❑ $W_n = 120\text{nm}$
- ❑ $W_p = 240\text{nm}$

45nm Sense Amplifier: Simulation

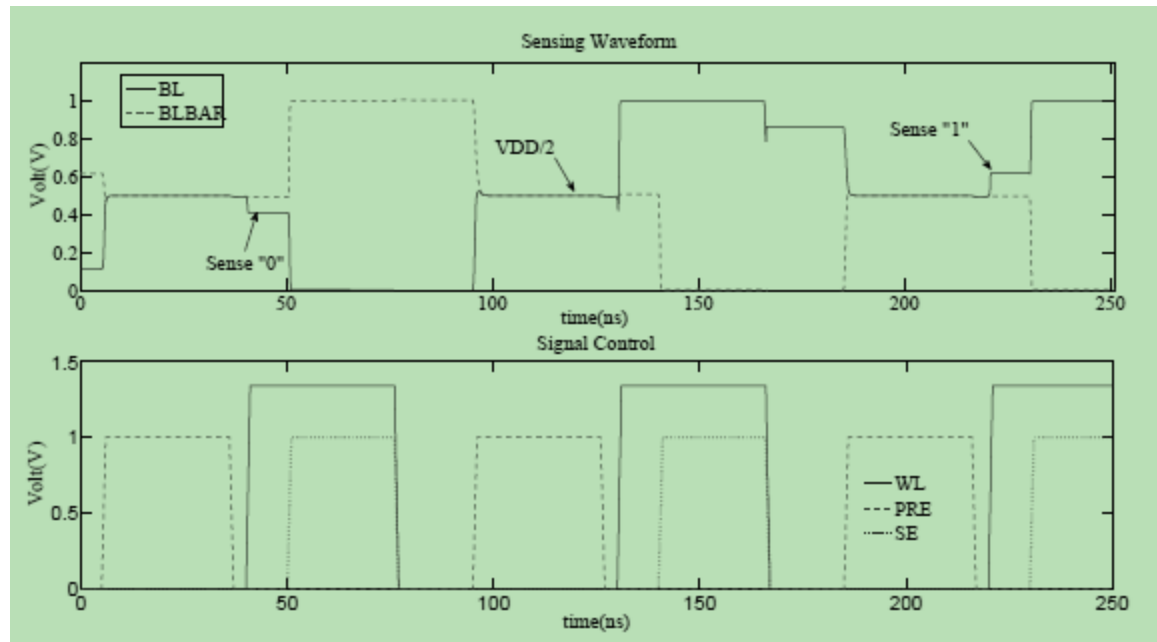

Design	Precharge time (ns)	Sense delay (ns)	Power, (μ W)	Sense Margin (mV)	Area (μm^2)
Schematic	10.31	1.79	1.84	26.91	-
Layout	10.40	1.91	1.88	26.86	6.045

45nm Sense Amplifier: Characterization of Optimal Design

Circuit	Precharge Time	Power Dissipation	Sense Delay	Sense Margin
Schematic	18.024 ns	1.166 μ W	7.460 ns	29.331 mV
Layout	18.20 ns	1.175 μ W	7.45 ns	29.256 mV
Dual- V_{th}	6.61 ns	0.941 μ W	3.476 ns	40.851 mV
Dual- T_{ox}	6.596 ns	0.895 μ W	3.464 ns	40.77 mV

A green light to greatness.

05/21/2013



UNT[®]

Sense Amplifier: Comparison

Research	Parameter	Feature	Approach	Result Improvement
Chow MWSCAS-2007	C_{BL}	Sense Speed	Spice simulations	Sense speed – 40%
Laurent TCASI 2002	C_{BL} , V_{th} , β	Signal Margin	Spice Simulations	-
Choudhary ISVLSI 2009	V_{th} , L, W	Yield	Monte Carlo analysis	Improved Yield
Singh TVLSI 2004		SE rise time	Spice simulations	Eliminated offset voltage
Our Sense Amplifier	Dual- V_{th} , T_{ox}	Process variability	Optimization	Sense delay – 54% Sense margin – 40% Average Power – 24%

Conclusions

- 35% of total energy in USA is consumed by electronics.
- Battery dependency is an critical constraint for portable systems.
- Energy efficient hardware, software at the same time better battery design needed for effective solutions.
- Smartphones need to have energy-efficient analog and RF components as WiFi and GSM communication consume significant portion of battery life.
- Energy-efficient level converters can perform better power management.
- 180 nm PLL design example consumed 90% less power.
- 45nm sense amplifier example consumed 24% less power.



Thank You !!!

Slides Available at:
<http://www.cse.unt.edu/~smohanty>